


12. For measuring voltage of any circuit, potentiometer is preferred to voltmeter because
- the potentiometer is cheap and easy to handle.
 - Calibration in the voltmeter is sometimes wrong.
 - The potentiometer almost draws no current during measurement.
 - Range of the voltmeter is not as wide as that of the potentiometer.
13. In the experiment of potentiometer, at balance point, there is no current in the
- main circuit
 - potentiometer circuit
 - galvanometer circuit
 - both main and galvanometer circuits
14. Sensitivity of potentiometer can be increased by
- increasing the E.m.f of the cell
 - increasing the length of the potentiometer
 - decreasing the length of the potentiometer wire
 - None of these
15. A cell has emf 2.8 V. It is connected to an external resistance of 5Ω . What will be the potential difference across the terminal of the cell, if its internal resistance is 2Ω .
- 0.28 V
 - 2V
 - 1.4V
 - 2.5V

16. Find the equivalent resistance between a and b

- $R/4$
- $R/2$
- R
- $2R$

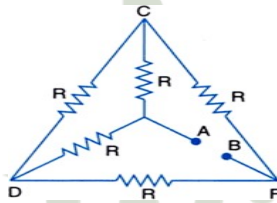17. A moving coil galvanometer can be converted into an ammeter by connecting to the moving coil galvanometer

- A low resistance in series
- A high resistance in series
- A low resistance in parallel
- A high resistance in parallel



18. A moving coil galvanometer can be converted into an ammeter by connecting to the moving coil galvanometer

- A low resistance in series
- A high resistance in series
- A low resistance in parallel
- A high resistance in parallel

19. The emf of battery A is balanced by a length of 75 cm on a potentiometer wire. The standard cell of emf 1.02 V is balanced by a length of 50 cm. The emf of cell A is,

- 1.25 V
- 1.35 V
- 1.53 V
- 2.05 V

20. AB is a wire of potentiometer with the increase in the value of resistance R, the shift in the balance point J will be

- Towards
- Towards A
- Remains constant
- First towards B then back towards A.

21. A potentiometer wire consists of a wire of length 4m and resistance 10 ohm. It is connected to a cell of emf 2V. The potential gradient of the wire is,

- 0.5 V/m
- 2 V/m
- 5 V/m
- 10 V/m

22. From the given diagram, Using Kirchoff's law, the value and actual direction of current I_x is:

- 2A and towards O
- 2A and same as in figure
- 2A and same as in figure
- 2A and towards O

