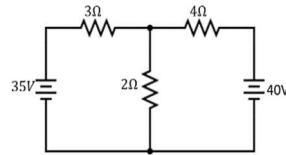


SAQs: (5 Marks questions)


1. Kirchhoff's law in electricity is very useful in solving the complicated circuit connections,

- What are the two basic Kirchhoff's laws?
- Using Kirchhoff's law of current and voltage, find the current through  $2\Omega$  resistor in the given circuit. [3]



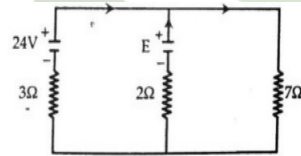
2. Kirchhoff's law in electricity is very useful in solving the complicated circuit connections,

- State and explain Kirchhoff's first law.
- What must be the emf  $E$  in the circuit so that the current flowing through the  $7\Omega$  resistor is  $1.80A$ ? (Ans:  $8.6V$ )



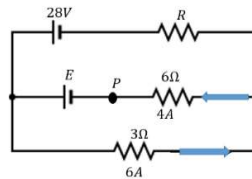3. Kirchhoff's laws are used in solving complex electrical circuit.

- Kirchhoff's laws are applicable to DC circuit. Is it applicable to AC circuit?
- Using Kirchhoff's law in electrical circuits, find,
  - The current in resistor  $R$
  - The unknown emf  $E$
  - The resistance  $R$
  - If the circuit is broken at  $P$ , what is the current in resistor  $R$ . [Ans:  $2A$ ,  $42V$ ,  $5\Omega$ ,  $3.5A$ ]



4. Wheatstone bridge is a good engineering of circuit designing. It has several uses and sometimes it shows problems in measuring resistance. [2+2+1]


- Write the balance condition Wheatstone bridge along with circuit diagram.
- Can we measure the internal resistance of a car battery with the help of Wheatstone bridge?
- Under what condition, Wheatstone bridge work perfectly.

5. Meter Bridge is usually used to determine the resistance of a wire segment and the comparison of two resistors. [1+3+1]

- On what principle does it work?
- In a meter bridge when the resistance in the left gap is  $3\Omega$  and an unknown resistance in the right gap, the balance point is obtained at  $40\text{ cm}$  from the


zero end. Find the value of unknown resistance. On shunting the unknown resistance with  $2\Omega$ , find the shift of the balance point on the bridge wire.

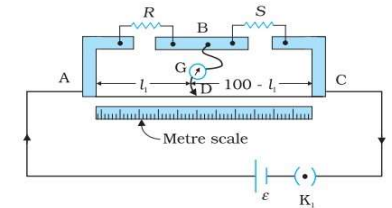- What happens if the meter bridge wire is made with copper wire?
6. a) In a meter bridge, the balance point is found to be at  $39.5\text{ cm}$  from the end  $A$ , when the resistor  $S$  is of  $12.5\Omega$ . Determine the resistance of  $R$ . Why are the connections between resistors in a Wheatstone or meter bridge made of thick copper strips? [2]



- Determine the balance point of the bridge above if  $R$  and  $S$  are interchanged. [1]
  - What happens if the galvanometer and cell are interchanged at the balance point of the bridge? [1]
7. a) State the principle of the Potentiometer. A potentiometer is also called a voltmeter of infinite resistance, why? [NEB 2080 (Model)]

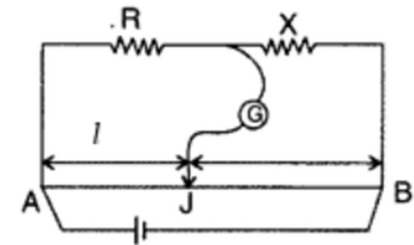- In the meter bridge experiment, the balance point was observed at  $J$  with  $l=20\text{cm}$ .
  - The values of  $R$  and  $X$  were doubled and then interchanged. What would be the new position of balance point?
  - If the galvanometer and battery are interchanged at the balance position, how will the balance point get affected?



8. (a) State the two Kirchhoff's laws for electrical circuits. [NEB 2080 (Model)]

- In Meter Bridge shown below, the null point is found at a distance of  $60.0\text{ cm}$  from  $A$ . If now a resistance of  $5\Omega$  is connected in series with  $S$ , the null point occurs at  $50\text{ cm}$ . Determine the values of  $R$  and  $S$ .

