

**To find internal resistance of a cell :**

The experimental arrangement to determine the internal resistance of a cell is shown in given figure. Here, we have to find the internal resistance ( $r$ ) of a test cell With Emf  $E$ .

During experiment, we slide a jockey over the potentiometer wire in order to obtain null deflection in the galvanometer. (Like meter bridge, the potentiometer also works under balanced condition).

**Step 1: When  $K_1$  is close and  $K_2$  is open:**

If  $C$  be the balanced point, then

$$\text{Emf: } E = V_{AC}$$

From principle of potentiometer,

$$V_{AC} \propto l_1$$

Thus,  $E \propto l_1$

$$\text{or, } E = kl_1 \dots\dots\dots (1)$$

**Step 2: When  $K_1$  is open and  $K_2$  is close:**

If  $C'$  be the balanced point, then

$$\text{TPD: } V = V_{AC'}$$

From principle of potentiometer,

$$V_{AC'} \propto l_2$$

Thus,  $V \propto l_2$

$$\text{or, } V = kl_2 \dots\dots\dots (2)$$


From equation (1) and (2),

$$\frac{E}{V} = \frac{l_1}{l_2}$$


$$\text{or, } \frac{Ir + IR}{IR} = \frac{l_1}{l_2}$$

$$\text{or, } \frac{r}{R} + 1 = \frac{l_1}{l_2}$$

$$\text{or, } r = \left[ \frac{l_1}{l_2} - 1 \right] \times R$$

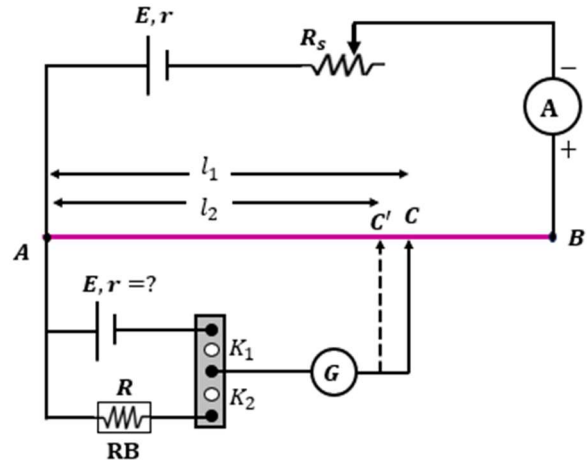

**Figure: Determination of internal resistance ( $r$ ) by using Potentiometer**

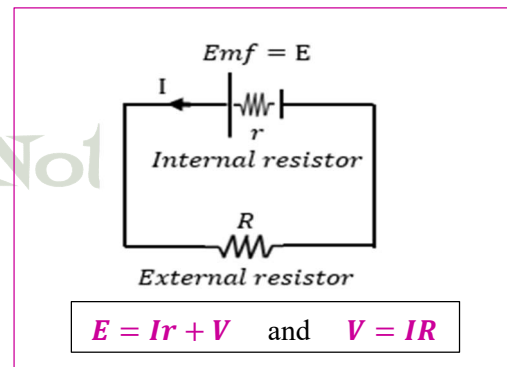

By knowing values of  $l_1$  and  $l_2$  and  $R$ , the internal resistance ( $r$ ) of the test cell can be calculated.

**Working formula:**

✓ For the comparison of emf of two cells:

If,  $l_1$  is balanced length in open circuit

$l_2$  is balanced length in close circuit

$R$  is the resistance shunted across the test cell (Connected across the test cell)

$$\text{Then, } r = \left[ \frac{l_1}{l_2} - 1 \right] \times R$$