

## TO DETERMINE THE RESISTANCE OF THE GIVEN WIRE BY USING METER BRIDGE AND HENCE FIND ITS RESISTIVITY (SPECIFIC RESISTANCE)

### APPARATUS REQUIRED:

- |                              |                               |
|------------------------------|-------------------------------|
| 1. Meter bridge              | 2. A wire (about 10 to 20 cm) |
| 3. A Micro meter screw gauge | 4. A resistance box           |
| 5. DC power source           | 6. Connecting wires           |
| 7. A galvanometer            | 8. A Jockey (slider)          |

### THEORY:

A meter bridge also called a **slide wire bridge** is an instrument that works on the principle of a Wheatstone bridge. A meter bridge is used in finding the unknown resistance of a wire. It is also used to compare the resistance of two wires.

### Construction of meter bridge

It consists of three copper ( $R = 0$ ) strips: A, B and C fixed on a wooden board. A standard resistance wire is fixed between the gap A and C. the wire is 1m long and has uniform cross-sectional area. A meter scale is fixed parallel to the wire. An unknown resistance  $X$  is fixed connected between the gap A and B. And a resistance box is connected between the gap B and C.

One terminal of a galvanometer is connected to point B and another terminal of the galvanometer is connected to a jockey (slider). We slide the jockey over the standard resistance wire in order to obtain null deflection in the galvanometer.

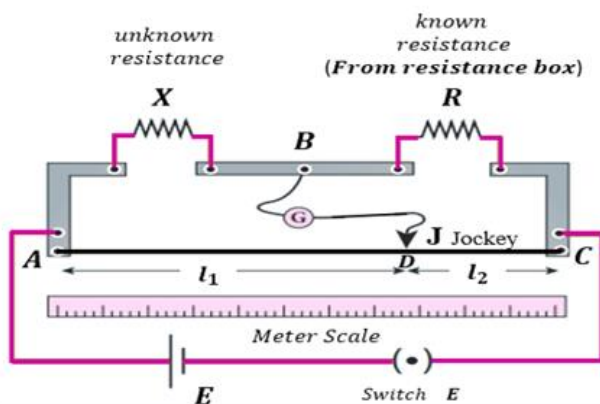


Figure (i): Circuit diagram to find unknown resistance using meter bridge

### Working of meter bridge:

The meter bridge works on the principle of Wheatstone bridge.

At balanced condition (as in figure (ii));

$$X \times Q = P \times R$$

$$\text{Or } X = \frac{P}{Q} \times R \dots \dots \dots (1)$$

For a wire of length  $l$  and cross-sectional area  $A$ ,

$$\text{the resistance } R \text{ is: } R = \rho \frac{l}{A}$$

For a wire of uniform thickness,  $R \propto l$

Therefore, in the given meter bridge;

$$P \propto l_1$$

$$\text{And, } Q \propto l_2$$

$$\therefore \frac{P}{Q} = \frac{l_1}{l_2} \dots \dots \dots (2)$$

Using equation (2) in equation (1), we get

$$X = \frac{l_1}{l_2} \times R \quad \left[ \text{Here, } l_2 = 100 - l_1 \right]$$

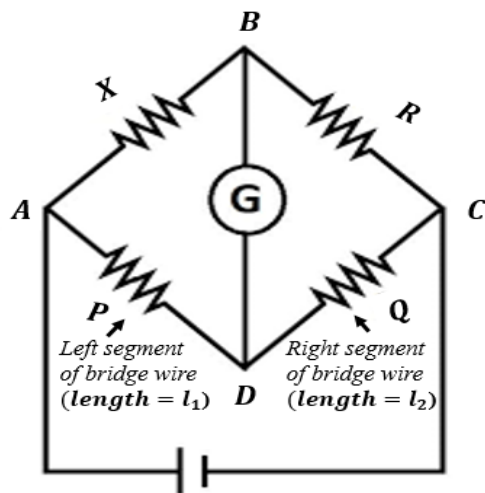


Figure (ii): Equivalent wheat stone bridge circuit

#### Note:

From above figures  
At balanced condition,

$$X \times Q = R \times P$$

OR

$$X \times l_2 = R \times l_1$$