

**TO COMPARE THE EMF'S OF TWO CELLS BY USING A POTENTIOMETER****APPARATUS REQUIRED:**

- |                     |                            |                     |
|---------------------|----------------------------|---------------------|
| 1. Potentiometer    | 2. DC Power Supply (2V-4V) | 3. Rheostat         |
| 4. Connecting wires | 5. Test cells (2 cells)    | 6. Three-way switch |
| 7. Galvanometer     | 8. Jockey                  |                     |

**THEORY:**

The potentiometer is an instrument used to measure the unknown voltage by comparing it with the known voltage. It can be used:

1. To determine the emf of a cell.
2. To determine the internal resistance of the given cell.
3. To compare the emf of different cells.

*[In measuring the emf of a cell, potentiometer is preferred over voltmeter.]*

**Construction of potentiometer:**

It consists of a long resistance wire (generally made of constantan or manganin) that is stretched on a wooden board. Usually, the potentiometer wire consists of 10 segments of uniform cross-section each of length 1m stretched on the wooden board. The wires are connected serially on the board by using metal strips.

**Principle of potentiometer:**

“When a constant current is passed through a wire (conductor) of uniform cross-sectional area, the potential drop across any segment of the wire is directly proportional to the length of the segment.”

$$i.e. \quad V \propto l$$

$$or, \quad V = K l$$

Here,  $K = \frac{V}{l}$  is called as potential gradient of potentiometer.

**Emf of a cell (E):**

The amount of work done in moving a unit positive charge from lower potential to higher potential inside a cell in an open circuit is called as its emf.

*The Potential difference (voltage) across a cell in an open circuit is called as the emf of the cell.*

**To compare the emfs of two cells:**

The experimental arrangement to compare emfs of two cells is shown in figure.

Here, we have to compare the emfs of two test cells having emf  $E_1$  and  $E_2$ .

During experiment, we slide a jockey over the potentiometer wire in order to obtain null deflection in the galvanometer. (Like meter bridge, the potentiometer also works under balanced condition).

**Step 1: When  $K_1$  is close and  $K_2$  is open:**

**Ohm's law:**  $V = IR$

$$V = I \frac{\rho l}{A}$$

$$V = \frac{I\rho}{A} l$$


$$V = K l$$

$$K = \frac{V}{l} \quad OR \quad K = \frac{I\rho}{A}$$

$K$  is called as **potential gradient**.

Unit of potential gradient:  $V/m$

**(Behaves as Least Count potentiometer)**

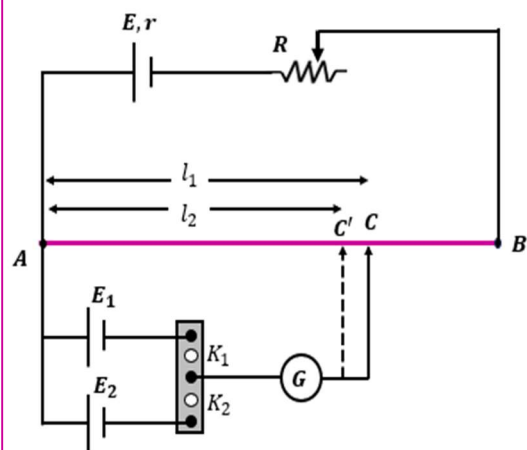

**Figure: Comparison of Emf of two cells ( $E_1:E_2$ ) using Potentiometer**