

TO DESIGN LOGIC GATES USING DIODES AND VERIFY THE TRUTH TABLES OF (I) OR GATE (II) AND GATE.

APPARATUS REQUIRED:

1. PN junction diodes
2. A light emitting diode (LED)
3. Battery- DC power supply [2V]
4. Bread board
5. Connecting wires
6. Jumpers
7. Resistors ($\sim 1K\Omega$)

THEORY:

The logic gates are the electronic circuits which give the logic decisions. A logic gate is a semiconductor device which performs logical operation on one or more binary inputs and produces a single binary output. Logic gates are built using diodes or transistors acting as electronic switches.

Boolean algebra:

Boolean algebra is a branch of mathematics that deals with operations on logical values with binary variables. The Boolean variables are represented as binary numbers to represent truths:

$$\begin{aligned} 1 &= \text{true (on ; high) and} \\ 0 &= \text{false (off ; low).} \end{aligned}$$

Elementary algebra deals with numerical operations whereas Boolean algebra deals with logical operations.

Truth table:

A truth table is a mathematical table used in logical analysis. A truth table has one or more columns for each input variable and one final column showing all possible results based on the relation.

OR gate:

The logic gate which gives high output when any of the inputs is high is called as OR gate.

Symbol:

An OR can have two or more inputs and a single output. However, in most of the cases, it has two inputs.

The symbol of OR gate is:



Fig. (a): Symbol of OR gate

Boolean Algebra:

If A and B are two inputs of OR gate, then the Output (Y) is given by:


$$Y = A + B$$

Truth table:

| Inputs | | Output |
|--------|---|-------------|
| A | B | $Y = A + B$ |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Fig. (b): Truth table of OR gate

Circuit Representation:

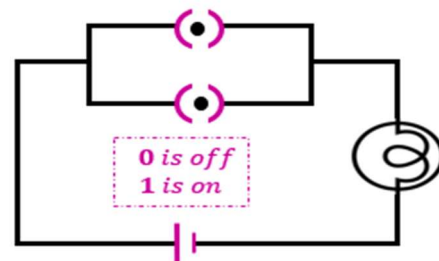

Circuit Representation of OR gate