

TO COMPARE THE RESISTANCE OF TWO GIVEN WIRES BY USING METER BRIDGE

APPARATUS REQUIRED:


1. Meter bridge
2. Two unknown resistance wires (about 10 - 20 cm)
3. DC power source
4. Connecting wires
5. A galvanometer
6. A Jockey (slider)

THEORY:

A meter bridge also called a **slide wire bridge** is an instrument that works on the principle of a Wheatstone bridge. A meter bridge is used in finding the unknown resistance of a wire. *It is also used to compare the resistance of two wires.*

Construction of meter bridge

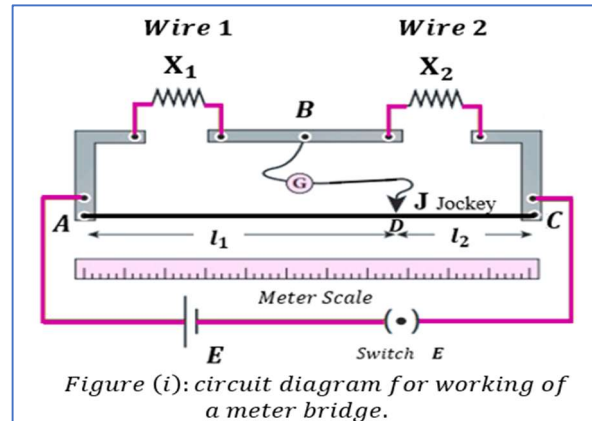It consists of three copper ($R = 0$) strips: A, B and C fixed on a wooden board. A standard resistance wire is fixed between the gap A and C. the wire is 1m long and has uniform cross-sectional area. A meter scale is fixed parallel to the wire. One unknown resistance wire X_1 is connected between the gap A and B. And another unknown resistance wire X_2 is connected between the gap B and C.



One terminal of a galvanometer is connected to point B and another terminal of the galvanometer is connected to a jockey (slider). We slide the jockey over the standard resistance wire in order to obtain null deflection in the galvanometer.

Working of meter bridge:

The meter bridge works on the principle of Wheatstone bridge.

At balanced condition (as in figure (ii));

$$X_1 \times Q = P \times X_2$$

$$\text{Or } \frac{X_1}{X_2} = \frac{P}{Q} \dots \dots \dots (1)$$

For a wire of length l and cross sectional area A ,

$$\text{the resistance } R \text{ is: } R = \rho \frac{l}{A}$$

For constant ρ and A , $R \propto l$

Therefore, in the given meter bridge;


$$P \propto l_1$$

$$\text{And, } Q \propto l_2$$

$$\therefore \frac{P}{Q} = \frac{l_1}{l_2} \dots \dots \dots (2)$$

Using equation (2) in equation (1), we get
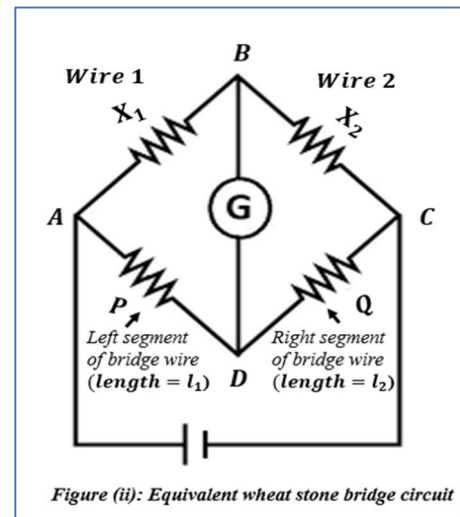
$$\frac{X_1}{X_2} = \frac{l_1}{l_2} \quad \text{[Here, } l_2 = 100 - l_1 \text{]}$$



Note:
From above figures
At balanced condition,
 $X_1 \times Q = P \times X_2$
OR
 $X_1 \times l_2 = X_2 \times l_1$